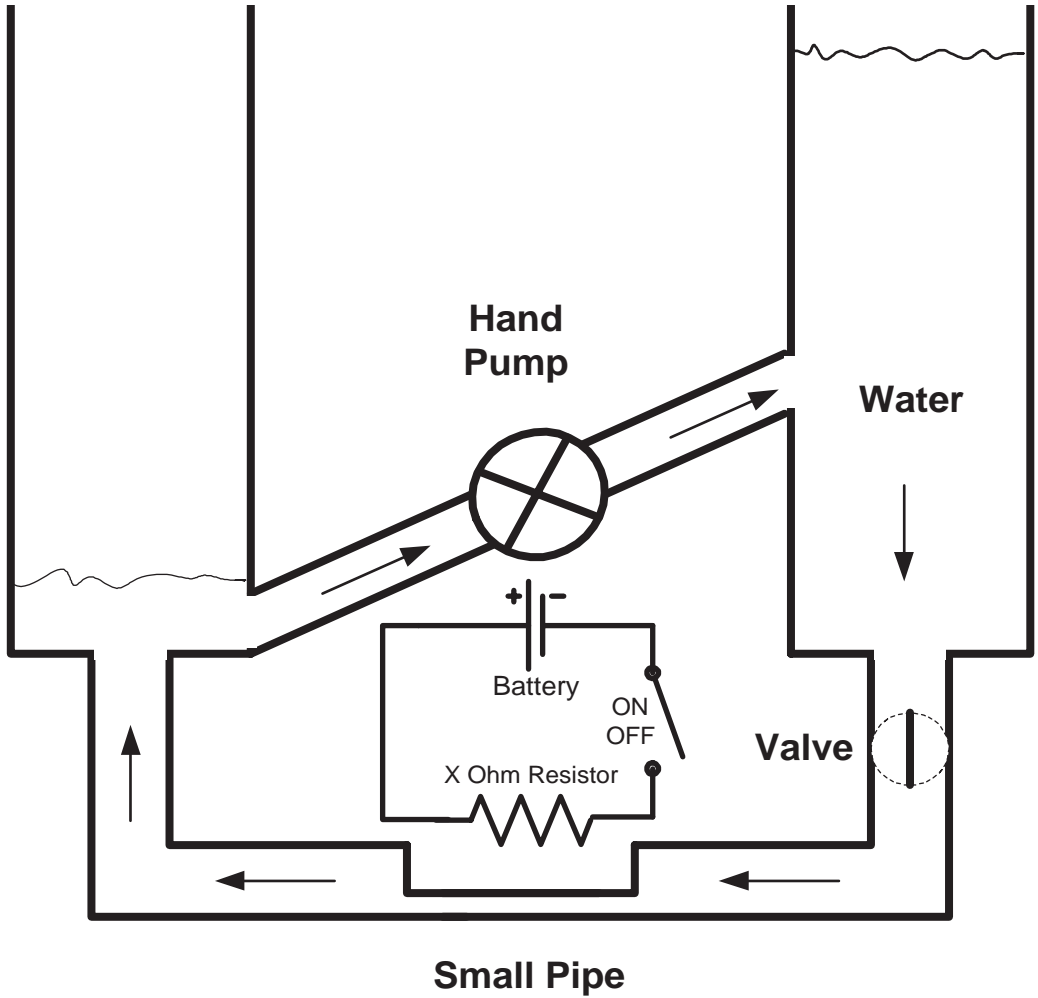


# How a Batteries Works

## An Electrical Circuit and its Water Analogy



Electrical ~ = Fluid Flow  
 Voltage ~ = Pressure  
 Current ~ = Particles/time  
 Resistance ~ = Pipe Resistance

Series Connection



Parallel Connection

